

CHAPTER 11

11-1 (a) $Z(s) = \frac{1}{\left(R_1 + \frac{1}{C \cdot s}\right)^{-1} + (L \cdot s + R_2)^{-1}}$

$Z(s) = \frac{(L \cdot s + R_2) \cdot (R_1 \cdot C \cdot s + 1)}{L \cdot C \cdot s^2 + (R_2 + R_1) \cdot C \cdot s + 1}$


By voltage division: $T_V(s) = \frac{R_2}{L \cdot s + R_2}$

(b) $R_1 := 2000 \quad R_2 := R_1$

$L := 0.1 \quad C := 0.25 \cdot 10^{-6}$

polyroots $\left(\begin{bmatrix} R_2 \\ L \end{bmatrix} \right) = -2 \cdot 10^4$ polyroots $\left[\begin{bmatrix} 1 \\ (R_1 + R_2) \cdot C \\ L \cdot C \end{bmatrix} \right] = \begin{bmatrix} -3.897 \cdot 10^4 \\ -1.026 \cdot 10^3 \end{bmatrix}$

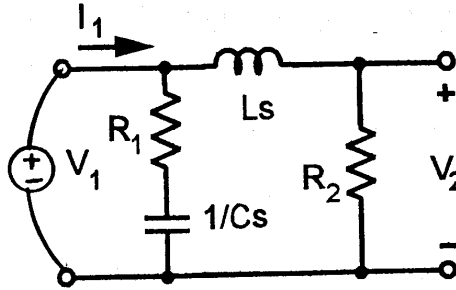$Z(s)$ has zeros at $s = R_2/L = -20000$ & $s = 1/R_1 \cdot C = -2000$ and poles at $s = -1026$ and -38970
 $T_V(s)$ has a pole at $s = -20000$



11-4 (a) $Z(s) = R_1 + \frac{1}{\frac{1}{L_1 \cdot s} + \frac{1}{R_2}}$

$Z(s) = \frac{[R_1 \cdot R_2 + (R_1 + R_2) \cdot L_1 \cdot s]}{(R_2 + L_1 \cdot s)}$


By current division: $I_2(s) = \frac{-L_1 \cdot s}{L_1 \cdot s + R_2} \cdot I_1(s)$

Hence $T_I(s) = \frac{I_2(s)}{I_1(s)} = \frac{-L_1 \cdot s}{L_1 \cdot s + R_2}$

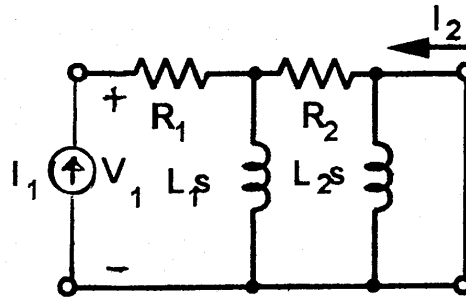(b) $R_1 := 500 \quad R_2 := 2000 \quad L_1 := 0.4$

polyroots $\left(\begin{bmatrix} R_2 \\ L_1 \end{bmatrix} \right) = -5 \cdot 10^3$ polyroots $\left[\begin{bmatrix} R_1 \cdot R_2 \\ (R_1 + R_2) \cdot L_1 \end{bmatrix} \right] = -1 \cdot 10^3$


$Z(s)$ has a zero at $s = -1000$ and a pole at $s = -5000$.
 $T_I(s)$ has a zero at $s = 0$ and a pole at $s = -5000$.



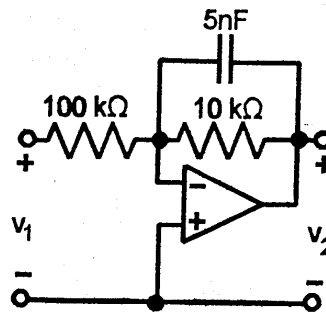11-7 $Z_2(s) = \frac{1}{5 \cdot 10^{-9} \cdot s + \frac{1}{10^4}} = \frac{2000 \cdot 10^5}{(s + 20000)}$ $Z_1(s) = 10^5$

$T_V(s) = \frac{Z_2}{Z_1} = \left[\frac{2000}{(s + 20000)} \right]$


$T_V(s)$ has a pole at $s = -20000$ and a zero at infinity



$$11-8 \quad Z_1(s) = \frac{1}{10^{-6} \cdot s + \frac{1}{5000}} = \frac{10^6}{(s+200)}$$

$$Z_2(s) = 10^4$$

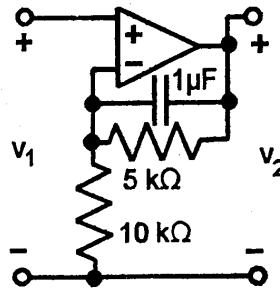
$$T_V(s) = \frac{Z_1 + Z_2}{Z_2} = \frac{10^4 + \frac{10^6}{s+200}}{10^4} = \frac{(s+300)}{(s+200)}$$



$T_V(s)$ has a zero at $s = -300$ and a pole at $s = -200$

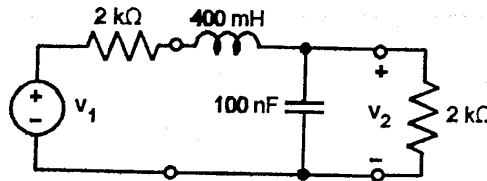11-13 By voltage division:

$$T_V(s) = \frac{\frac{1}{10^{-7} \cdot s + 5 \cdot 10^{-4}}}{\frac{1}{10^{-7} \cdot s + 5 \cdot 10^{-4}} + 0.4 \cdot s + 2000}$$




$$T_V(s) = \frac{25000000}{(s^2 + 10000 \cdot s + 50000000)}$$

$$h(t) = L^{-1} \left[5000 \cdot \left[\frac{5000}{(s+5000)^2 + 5000^2} \right] \right] = 5000 \cdot e^{-5000t} \cdot \sin(5000 \cdot t) \cdot u(t)$$

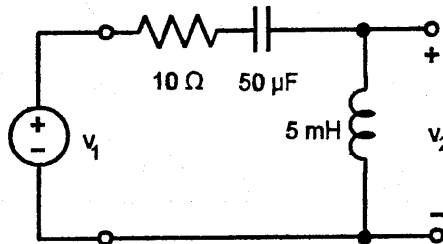11-15 By voltage division:

$$T_V(s) = \frac{5 \cdot 10^{-3} \cdot s}{5 \cdot 10^{-3} \cdot s + (50 \cdot 10^{-6} \cdot s)^{-1} + 10}$$

$$T_V(s) = \frac{s^2}{s^2 + 2000 \cdot s + 4000000}$$




$$h(t) = L^{-1} \left(\frac{s^2}{s^2 + 2000 \cdot s + 4000000} \right) = L^{-1} \left[1 - \frac{2000 \cdot (s+1000)}{(s+1000)^2 + (1000 \cdot \sqrt{3})^2} - \frac{2000}{\sqrt{3}} \cdot \frac{1000 \cdot \sqrt{3}}{(s+1000)^2 + (1000 \cdot \sqrt{3})^2} \right]$$

$$h(t) = \delta(t) - \left(\frac{2000}{\sqrt{3}} \cdot \exp(-1000 \cdot t) \cdot \sin(1000 \cdot \sqrt{3} \cdot t) + 2000 \cdot \exp(-1000 \cdot t) \cdot \cos(1000 \cdot \sqrt{3} \cdot t) \right) \cdot u(t)$$

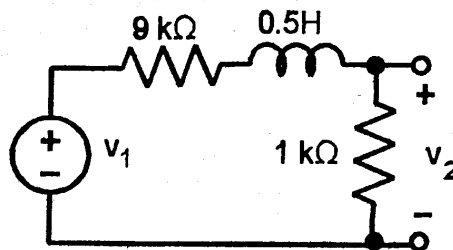11-21 By voltage division:

$$T_V(s) = \frac{1000}{1000 + 0.5 \cdot s + 9000} = \frac{2000}{(s+20000)}$$

$$g(t) = L^{-1} \left[\frac{2000}{(s+20000)} \cdot 1 \right] = 0.1 \cdot (1 - e^{-20000 \cdot t}) \cdot u(t)$$




11-23 By voltage division:

$$T_V(s) = \frac{\frac{1}{10^{-7} \cdot s + 5 \cdot 10^{-4}}}{\frac{1}{10^{-7} \cdot s + 5 \cdot 10^{-4}} + 0.4 \cdot s + 2000}$$


$$T_V(s) = \frac{25000000}{(s^2 + 10000 \cdot s + 50000000)}$$

$$G(s) = \frac{T_V}{s} = \frac{25000000}{s(s+5000+j \cdot 5000)(s+5000-j \cdot 5000)} = \frac{1}{s} = \frac{(-.25 - .25j)}{s(s+5000+5000j)} + \frac{(-.25 + .25j)}{(s+5000-5000j)} + \frac{.5}{s}$$

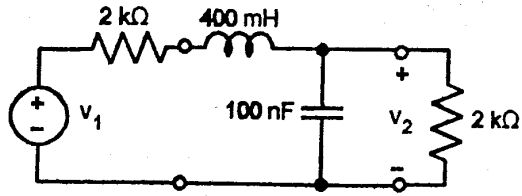
$$g(t) = \left(0.5 \sqrt{2} \cdot \exp(-5000 \cdot t) \cdot \cos\left(5000 \cdot t + 3 \cdot \frac{\pi}{4}\right) + 0.5 \right) \cdot u(t)$$



11-63(a) C1 is an inverting amplifier

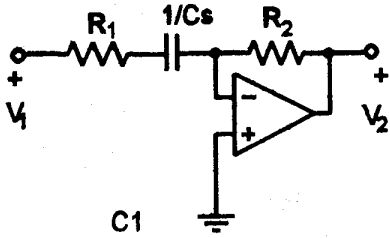

C2 is a noninverting amplifier

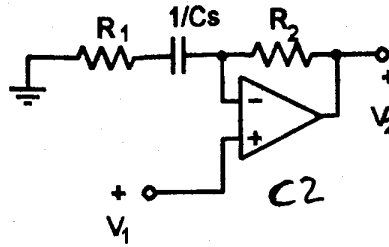

For both circuits: $Z_1 = R_1 + \frac{1}{C \cdot s} = \frac{R_1 \cdot C \cdot s + 1}{C \cdot s}$

and $Z_2 = R_2$

For C1: $T_V(s) = \frac{Z_2}{Z_1} = \frac{-R_2 \cdot C \cdot s}{R_1 \cdot C \cdot s + 1}$

For C2: $T_V = \frac{Z_1 + Z_2}{Z_1} = \frac{(R_1 + R_2) \cdot C \cdot s + 1}{R_1 \cdot C \cdot s + 1}$

Pole at $s = -\frac{1}{R_1 \cdot C}$, zero at $s = 0$

Pole at $s = -\frac{1}{R_1 \cdot C}$, zero at $s = -\frac{1}{(R_1 + R_2) \cdot C}$



(b) Use C1 in cascade with C2 $T(s) = \frac{-s \cdot (s + 300)}{(s + 200) \cdot (s + 400)} = T_{C1} \cdot T_{C2} = \left[\frac{-\frac{3 \cdot s}{800}}{\frac{s}{200} + 1} \right] \left[\frac{\frac{s}{300} + 1}{\frac{s}{400} + 1} \right]$

For C1: $T_{C1} = \frac{-R_2 \cdot C \cdot s}{R_1 \cdot C \cdot s + 1} = \frac{-\frac{3 \cdot s}{800}}{\frac{s}{200} + 1}$

Let $C := 10^{-7}$ $R_1 := \frac{1}{200 \cdot C}$ $R_2 := \frac{3}{800 \cdot C}$
 $R_1 = 5 \cdot 10^4$ $R_2 = 3.75 \cdot 10^4$

For C2: $T_{C2} = \frac{(R_1 + R_2) \cdot C \cdot s + 1}{R_1 \cdot C \cdot s + 1} = \frac{\frac{s}{300} + 1}{\frac{s}{400} + 1}$

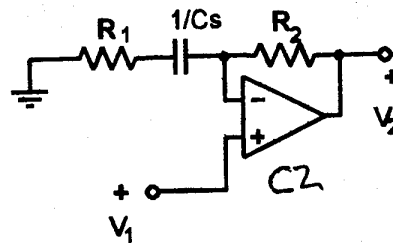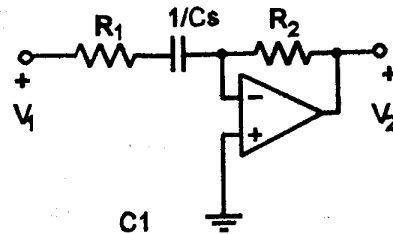Let $C := 10^{-7}$ $R_1 := \frac{1}{400 \cdot C}$ $R_2 := \frac{1}{300 \cdot C} - R_1$
 $R_1 = 2.5 \cdot 10^4$ $R_2 = 8.333 \cdot 10^3$



(c) C1 and C2 produce zeros closer to the s-plane origin than their poles. $T_3 = \frac{s(s + 500)}{(s + 200) \cdot (s + 400)}$

can not be realized. It requires a zero at $s = -500$ which is further from the origin than either pole.

(d) To be realizable using C1 and C2 it must be possible to partition $T(s)$ into first order factors each of which has a zero closer to the origin than its pole.

11-65 (a) Using voltage division in the RLC ckt

$$T_V(s) = \frac{L \cdot s}{R + \frac{1}{C \cdot s} + L \cdot s} = \frac{L \cdot C \cdot s^2}{L \cdot C \cdot s^2 + R \cdot C \cdot s + 1}$$

$$\omega_0 = \frac{1}{\sqrt{L \cdot C}} \quad \text{and} \quad \zeta = \frac{R}{2} \cdot \sqrt{\frac{C}{L}}$$

Using node analysis in the RC OP AMP ckt

$$\begin{bmatrix} C_1 \cdot s + C_2 \cdot s + \frac{1}{R} & -\left(C_2 \cdot s + \frac{1}{R}\right) \\ -C_2 \cdot s & C_2 \cdot s + \frac{1}{R} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} C_1 \cdot s \cdot V_1 \\ 0 \end{bmatrix}$$

$$\Delta(s) = \frac{R^2 \cdot C_1 \cdot C_2 \cdot s^2 + (R \cdot C_1 + R \cdot C_2) \cdot s + 1}{R^2}$$

$$\Delta_B(s) = C_1 \cdot C_2 \cdot s^2 \cdot V_1$$

$$T_V(s) = \frac{R^2 \cdot C_1 \cdot C_2 \cdot s^2}{R^2 \cdot C_1 \cdot C_2 \cdot s^2 + (R \cdot C_1 + R \cdot C_2) \cdot s + 1}$$

$$\omega_0 = \frac{1}{R \cdot \sqrt{C_1 \cdot C_2}} \quad \text{and} \quad \zeta = \frac{1}{2} \left(\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}} \right)$$

(b) For the RLC ckt $L \cdot C = 10^{-12}$ $R \cdot \sqrt{\frac{C}{L}} = 1$ Let $C = 10^{-8}$ Then $L = 10^{-4}$ $R = 100$

For the RC OP AMP ckt $C_1 \cdot C_2 \cdot R^2 = 10^{-12}$ $\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}} = 1$

The expression $\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}}$ is of the form $f(x) = x + \frac{1}{x}$, whose minimum value is $f(x) = 2$ at $x = 1$

Therefore the RC OP AMP circuit can not produce $\zeta = 0.5$.


Choose the RLC circuit since its element values are reasonable and it meets the specification.

(c) For the RLC ckt $L \cdot C = 10^{-4}$ $R \cdot \sqrt{\frac{C}{L}} = 4$ Let $C = 10^{-6}$ then $L = 100$ $R = 4 \cdot 10^4$


For the RC OP AMP ckt: Let $R = 10^4$, Assume: $C_1 := 10^{-6}$ $C_2 := 2 \cdot C_1$

Given $C_1 \cdot C_2 \cdot 10^8 = 10^{-4}$ $\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}} = 4$ Find $(C_1, C_2) = \begin{bmatrix} 2.679 \cdot 10^{-7} \\ 3.732 \cdot 10^{-6} \end{bmatrix}$ many other solutions are possible

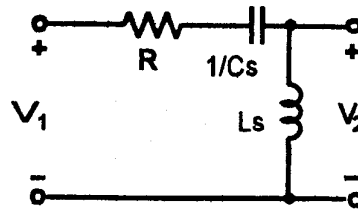The RLC circuit requires $L = 100$ H which is too large to be practical. Choose the RC OP AMP circuit.



C1

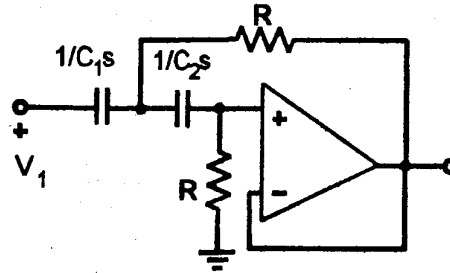

C2